

Stepper Motor Driving With Peripheral Drivers (Driver ICs)

*Michael Schultis**HVAL – Standard Linear and Logic*

ABSTRACT

This application report describes in detail how to interface stepper motors with TI peripheral drivers. Primarily, this report discusses how to connect and drive stepper motors, including the stepper motor driving patterns. Advantages and disadvantages to each stepping pattern are discussed; and logic tables, timing diagrams, and pictorial representations of each driving pattern are provided.

Contents

1	Peripheral Driver (Driver IC) Overview.....	2
2	Stepper Motors.....	2
2.1	Unipolar Stepper Motors.....	2
2.2	Bipolar Stepper Motors.....	3
3	Stepper Motor Driving Overview.....	4
3.1	Unipolar Stepper Motor Driving Block Diagram.....	4
3.2	Detailed Design Considerations.....	4
3.3	Bipolar Stepper Motor Driving Block Diagram.....	5
3.4	Detailed Design Considerations.....	5
4	Stepper Motor Driving Patterns.....	6
4.1	Wave Drive Operation.....	6
4.2	Full-Step Operation.....	7
4.3	Half-Step Operation.....	8

1 Peripheral Driver (Driver IC) Overview

A peripheral driver is a type of integrated circuit (IC) that can be used to drive relays, solenoids, stepper motors, LEDs, and other peripherals. These peripheral driver ICs are typically described as high-voltage, high-current Darlington transistor arrays, multi-channel relay and inductive load sink drivers, or quadruple Half-H drivers.

Peripheral Drivers are useful for driving both low and high voltage peripherals within appliance, HVAC, automotive, telecom, and other applications.

The BOOSTXL-ULN2003 BoosterPack can be paired with an MSP430 Launchpad (ti.com/launchpad) to drive stepper motors and help understand stepper motor driving patterns. See <http://www.ti.com/tool/boostxl-uln2003> for additional information including hardware evaluation and software examples.

2 Stepper Motors

There are two types of stepper motors: the unipolar stepper motor and the bipolar stepper motor. A unipolar stepper motor has current flowing through each of the coils in a single direction, and the bipolar stepper motor has current flowing in both directions of the coil.

2.1 Unipolar Stepper Motors

Unipolar stepper motors only require current to flow in a single direction, which makes hardware design simpler because only a low side switch/driver is required (a switch to conduct current to ground from the component - see [Figure 1](#)). The high-side of the motor phase is connected directly to the supply voltage without a switch. Unipolar stepper motors can be driven by a stepper motor sequence using a peripheral driver - [ULN2003A](#) and [TPL7407L](#) are examples of devices that can drive these stepper motors. See [Section 3.1](#) for additional information regarding how to connect a stepper motor to a peripheral driver.

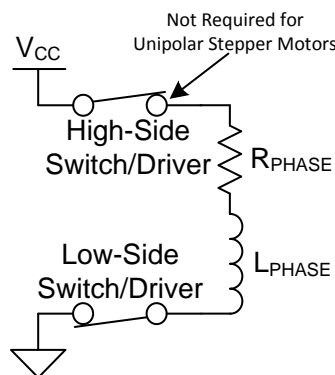


Figure 1. Low-Side and High-Side Switches/Drivers

Unipolar stepper motors come in three primary wiring configurations, 5-wire, 6-wire, and 8-wire, where 5-wire and 6-wire stepper motors are the most common. In a 5-wire stepper motor the center tap connections are shorted together internally as shown in [Figure 2](#). In a 6-wire stepper motor the center tap connections are separate connections as shown in [Figure 3](#). A 6-wire stepper motor can effectively act as a 5-wire stepper motor by connecting the two center tap wires.

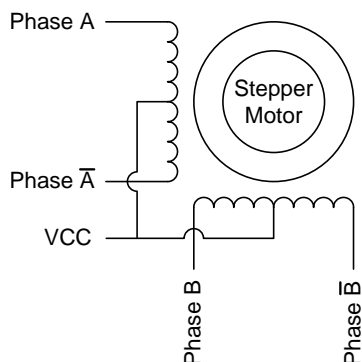


Figure 2. 5-Wire Unipolar Stepper Motor

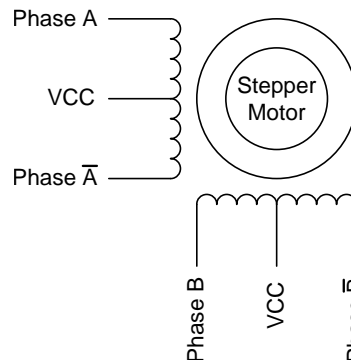


Figure 3. 6-Wire Unipolar Stepper Motor

2.2 Bipolar Stepper Motors

Bipolar stepper motors require both a low-side driver and a high-side driver (see [Figure 4](#)). This allows the coils to be biased in both directions, requiring two Half-H drivers (one Full-H bridge). The [L293D](#) is an example of a device that can drive these types of stepper motors, see [Section 3.1](#) for additional information.

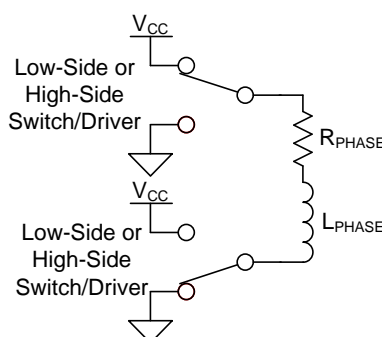


Figure 4. Variable Low-Side and High-Side Switches/Drivers

Bipolar stepper motors only come in a 4-wire configuration and do not have center tap connections. See [Figure 5](#) for the wiring of the bipolar stepper motor.

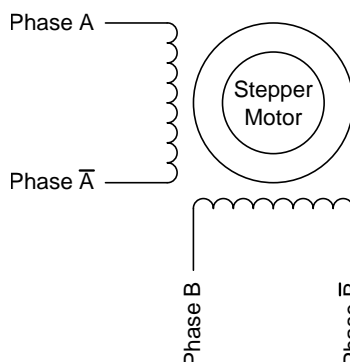


Figure 5. 4-Wire Bipolar Stepper Motor

3.3 Bipolar Stepper Motor Driving Block Diagram

A common application for peripheral drivers is driving bipolar stepper motors. Figure 7 shows in detail a typical block diagram for driving a bipolar stepper motor using an L293D or a similar peripheral driver device such as SN754410.

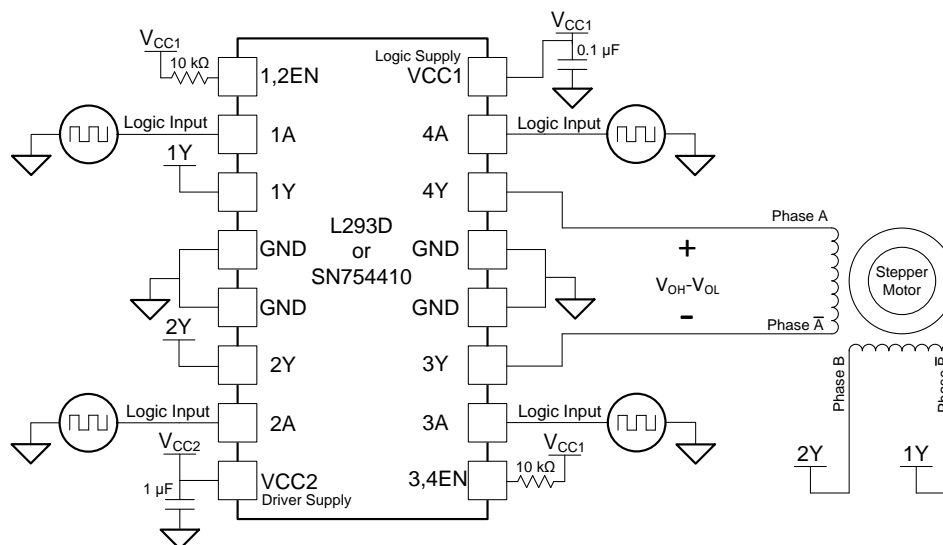


Figure 7. Driving a Bipolar Stepper Motor

3.4 Detailed Design Considerations

When using a peripheral driver for stepper motor driving applications there are a few design considerations that should be highlighted.

1. V_{CC1} and V_{CC2} should be within the acceptable recommended voltage range - see device Electrical Characteristics for further information.
2. Logic Inputs should be within the acceptable recommended voltage range - see device Electrical Characteristics for further information.
3. The current through each motor phase (I_{phase}) is a function of the high-level output voltage (V_{OH}), the low-level output voltage (V_{OL}) and the phase resistance (R_{phase})
 - Equation 2 provides the equation for the Relay Current
 - See device Electrical Characteristics for the maximum allowable continuous output current per channel (I_O), high-level output voltage (V_{OH}), and low-level output voltage (V_{OL})

$$I_{phase} = \frac{V_{OH} - V_{OL}}{R_{phase}} \quad (2)$$

4 Stepper Motor Driving Patterns

There are multiple methods to driving stepper motors, each with their own advantages and disadvantages. The sections below describe each method as well as their advantages and disadvantages.

4.1 Wave Drive Operation

The Wave Drive mode of operation is typically considered to be the most simple way of driving a stepper motor, but is also the least common mode of stepper motor driving, due to its shortfalls relative to Full-Step (torque) and Half-step (precision) patterns. The wave drive mode would likely be used in applications where reduced power consumption is important and high torque is unnecessary. Because of its simplicity, it is easiest to help discuss the functional operation of stepper motors.

For this mode of operation, each phase of the motor is activated in succession with only a single phase being activated at any point in time. Figure 8 and Figure 9 describe the step pattern required for the wave drive method, while Figure 10 provides a pictorial representation of the motor steps. Depending on the motor, each step in the sequence will rotate a defined angular distance. Figure 10 represents a motor with 4 steps per revolution, but many common stepper motors will have 32 or 64 steps per revolution; furthermore, others can have even higher precision. Each step for the motor in Figure 10 spins the motor 90°. As each phase is activated in succession, the permanent magnet on the rotor is attracted to the activated coil in the stator.

		Step Sequence			
		1	2	3	4
Motor Phase	A	1	0	0	0
	B	0	1	0	0
	\bar{A}	0	0	1	0
	\bar{B}	0	0	0	1

Figure 8. Wave Drive Logic Table

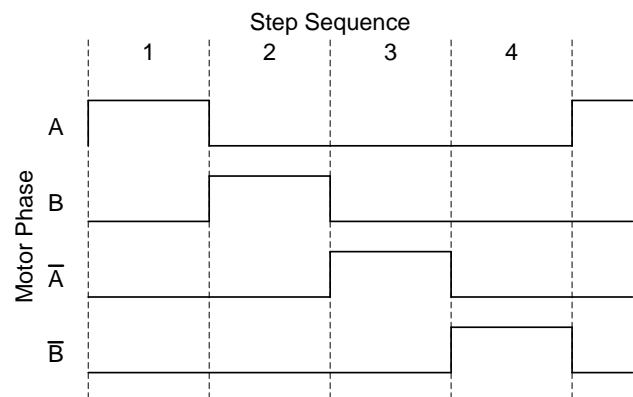


Figure 9. Wave Drive Timing Diagram

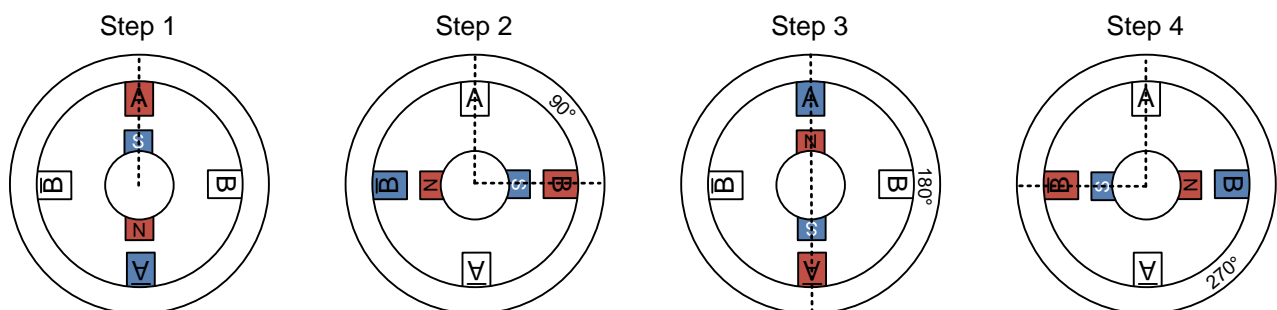


Figure 10. Wave Drive Motor Coil Sequence

4.2 Full-Step Operation

The full-step mode of operation is the most commonly used way to drive a stepper motor, as it has improved torque over the wave drive method and constant torque relative to the half-step method. The wave drive mode would likely be used in applications where increased torque is required.

For this mode of operation, two phases of the motor are activated simultaneously to provide an additional attractive force relative to the wave drive method, while still maintaining the resolution of the wave drive method. Figure 11 and Figure 12 describe the step pattern required for the full-step method, while Figure 13 provides a pictorial representation of the motor steps. Depending on the motor, each step in the sequence will rotate a defined angular distance. Figure 13 represents a motor with 4 steps per revolution, but many common stepper motors will have 32 or 64 steps per revolution; furthermore, others can have even higher precision. Each step for the motor in Figure 13 spins the motor 90°. Note that the full-step method has the stator attracted to a space between each of the phases that are activated, as opposed to the wave drive method where the stator is attracted directly to the activated phase. Because the stator is attracted to a space between two phases, there is a point where the two phases are pulling in opposite directions. As a consequence the full-step method does not provide torque twice that of the wave-drive method (despite twice the power consumption), but rather more equivalent to 1.4x the wave drive method.

		Step Sequence			
		1	2	3	4
Motor Phase	A	1	0	0	1
	B	1	1	0	0
	\bar{A}	0	1	1	0
	\bar{B}	0	0	1	1

Figure 11. Full-Step Logic Table

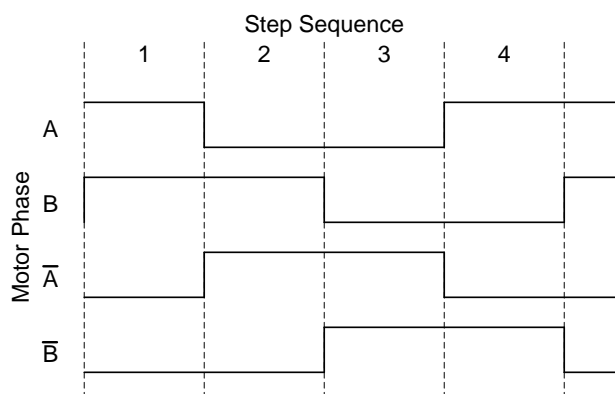


Figure 12. Full-Step Timing Diagram

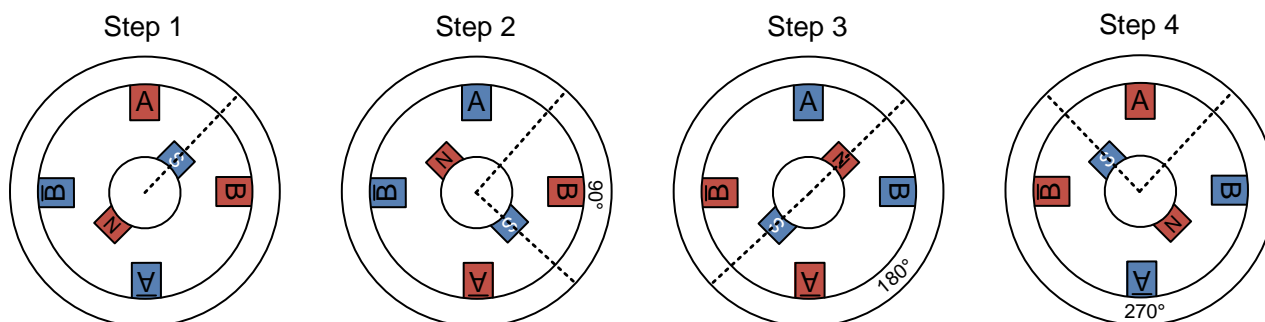


Figure 13. Full-Step Motor Coil Sequence

4.3 Half-Step Operation

The half-step mode of operation is less commonly used compared to the full-step method, but is typically more common than the wave drive method, as it enables better stepper resolution with the same motor. One disadvantage to the half-step method is that the torque swings between that of the wave drive method and that of the full-step method. Some devices, however, have internal circuitry to limit current and reduce torque ripple when half-stepping. The half-step mode would likely be used in applications where increased resolution is required.

For this mode of operation, two phases of the motor are activated simultaneously followed by a single phase. This ultimately provides additional resolution relative to both the wave drive and full-step methods. Figure 14 and Figure 15 describe the step pattern required for the half-step method, while Figure 16 provides a pictorial representation of the motor steps. Depending on the motor, each step in the sequence will rotate a defined angular distance. Figure 16 represents a motor with 4 steps per revolution, but many common stepper motors will have 32 or 64 steps per revolution; furthermore, others can have even higher precision. Each step for the motor in Figure 16 spins the motor 45°. Note that the half-step method allows for twice the resolution of the full-step method because each step is half that of the full-step method.

		Step Sequence							
		1	2	3	4	5	6	7	8
Motor Phase	A	1	1	0	0	0	0	0	1
	B	0	1	1	1	0	0	0	0
	\bar{A}	0	0	0	1	1	1	0	0
	\bar{B}	0	0	0	0	0	1	1	1

Figure 14. Half-Step Logic Table

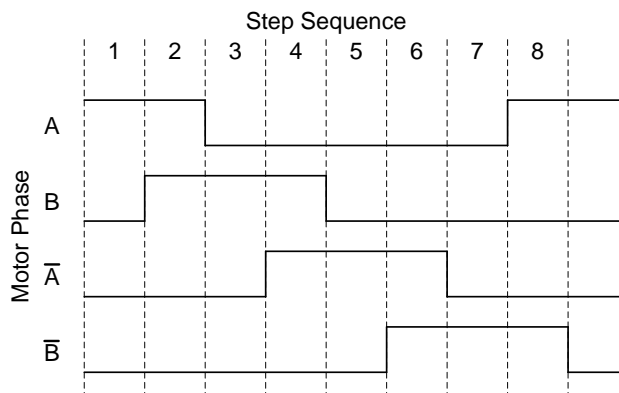


Figure 15. Half-Step Timing Diagram

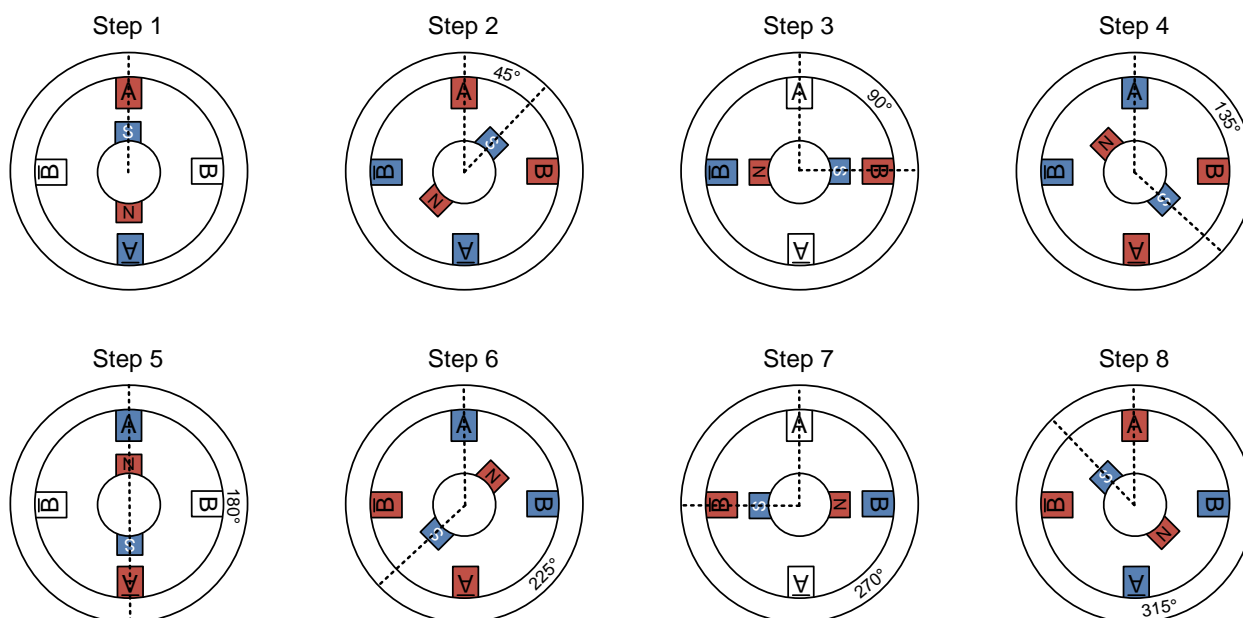


Figure 16. Half-Step Motor Coil Sequence

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com